

Weekly Test - 05
Subject : Digital Logic
Topic : Sequential Circuit



Time Duration - 50 Min


Maximum Marks - 20

Note : Negative Marking - 1/3, NAT no negative marking

{For MSQs no part marking no negative marking(from week onwards)}

 
Part A : 1 to 6 questions each will carry 1 marks (MCQs + NAT)

- If the 5-bit ripple counter and 5-bit synchronous counter are having flip-flops with a propagation delay of 40 ns, then the total sum ($x + y$) of maximum delay in the ripple counter (x) and synchronous counter (y) will be _____(in ns)
- If the J-input of a J-K flip-flop is treated as input and an inverter is connected between J and K inputs, the J-K flip-flop becomes
 - D Latch
 - D Flip Flop
 - T Flip Flop
 - JK Flip Flop
- Determine f_{\max} for the 4-bit parallel carry synchronous counter, if t_{pd} for each flip-flop is 40ns and t_{pd} for each AND gate is 10ns
 - 2 MHz
 - 0.2 MHz
 - 20 MHz
 - 25 MHz
- The two negative edge triggered D flip flops are interconnected as shown below. Assume initially $Q_1Q_0=00$. The outputs Q_1Q_0 of the circuit, will be




- 00, 01, 10, 11, 00
- 00, 01, 11, 10, 00
- 00, 11, 10, 01, 00
- 00, 10, 11, 01, 00

 - How many different output states the following circuit is having?



 
- Various types of counters are cascaded as shown below. The signal available at output Y will have the frequency.



- 20Hz
- 10Hz
- 320Hz
- 160Hz


Part B: 7 to 13 questions each will carry 2 marks (MCQs + NAT)

 7. If the $Q_a Q_b$ of counter shown below at clock time t_n is 10, then the state $Q_a Q_b$ of counter at t_{n+3} (after 3 clock cycles) will be



- (a) 00 (b) 01
(c) 10 (d) 11

 8. Figure shows a mod-K counter, Here K is equal to



- (a) 1 (b) 2
(c) 3 (d) 4

9. Consider the following conditions:


1. $t_p < \Delta t$ 2. $\Delta t < T$ 3. $t_p > \Delta t$ 4. $\Delta t < T$

Consider the following conditions:

Where t_p = pulse width, Δt = propagation delay of flip-flop and T = clock period. The race around condition in the flip-flop can be avoided if conditions_____


- (a) 1 and 2 are correct
(b) 1, 3 and 4 are correct
(c) 2 and 3 are correct
(d) 2, 3 and 4 are correct

 10. In the NAND latch shown below, initially $A = B = 1$ and then B is replaced by a sequence 10 10 10, the outputs X and Y will be (assume initially $X = 0$ and $Y = 1$)




- (a) fixed at 0 and 1 respectively
(b) fixed at 1 and 0 respectively
(c) $X = 1010\dots$ and $Y = 0101$
(d) $X = 0101\dots$ and $Y = 1010$

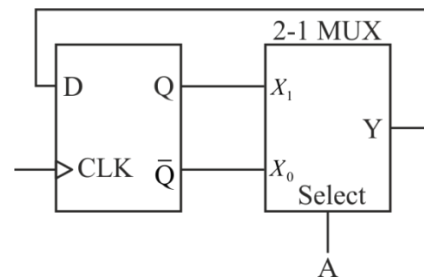11. The state transition diagram for the logic circuit shown is



- (a) (b) (c) (d)

 12. A circuit for truncated ripple counter together with a reset function labelled y , is shown below.



Then the reset function y can be expressed as

- (a) $y = Q_3(Q_2 + Q_1)$
- (b) $y = Q_3 + Q_2Q_1$
- (c) $y = \overline{Q_3(Q_2 + Q_1)}$
- (d) $y = \overline{Q_3 + Q_2Q_1}$

13. A 6 bit counter is designed with a switch S . Function of switch S is to switch the counter from up counter to down counter and vice-versa after MOD-no. of clock pulses irrespective of starting state of counter. Counter started with state $(101100)_2$ in up-counter mode then after how many clock-pulses it will be at $(110010)_2$ in down-mode condition of the switch _____.

Answer Key

- | | |
|----------|-----------|
| 1. (240) | 8. (c) |
| 2. (b) | 9. (a) |
| 3. (c) | 10. (a) |
| 4. (b) | 11. (d) |
| 5. (6) | 12. (a) |
| 6. (b) | 13. (122) |
| 7. (c) | |



For more questions, kindly visit the library section: Link for web: <https://smart.link/sdfez8ejd80if>



PW Mobile APP: <https://smart.link/7wwosivoicgd4>