

## Weekly Test - 04

### Digital Logic



**Time Duration - 50 Min**

**Maximum Marks - 20**

**Note :** Negative Marking - 1/3, NAT no negative marking

{For MSQs no part marking no negative marking( from week onwards)}

**Part A : 1 to 6 questions each will carry 1 marks (MCQs + NAT)**

1. [NAT]

We have two types of digital units available:


2 : 1 MUX  $\rightarrow$  Cost 2 unit each

NOT gate  $\rightarrow$  Cost 1 unit each

We have to implement half subtractor circuit then the minimum costing required to implement the circuit is \_\_\_\_\_ unit.

 2. [NAT]


A 3 : 8 decoder circuit is as given below :



When applied input is  $ABC = (110)_2$  then the sum of output pin numbers which will glow will be (\_\_\_\_\_) <sub>10</sub>.

[MCQ]

 3. The latching action of a latch shown below, is controlled by two inputs  $X_1$ ,  $X_2$ . The invalid input combinational  $X_1$ ,  $X_2$  will be



- (a)  $X_1 = 1, X_2 = 0$       (b)  $X_1 = 0, X_2 = 1$   
 (c)  $X_1 = X_2 = 0$       (d)  $X_1 = X_2 = 1$


4. [NAT]

Two numbers A & B are 2-bit numbers i.e.  $A = a_1, a_0$  &  $B = b_1, b_0$ . If we perform operation  $(A - B)$  using parallel subtractor with minimum no. of possible gates XOR, AND, OR, NOT etc. then minimum number of 2-input XOR gate required will be \_\_\_\_\_.

5. [MCQ]

The design of a combinational circuit is attempted as demonstrated below.

 - (i) For  $S = 0$ ,  $y = 0$  regardless of status of B  
 (ii) For  $S = 1$  and  $B = 0$ ,  $y = x_1$   
 (iii) For  $S = 1$  and  $B = 1$ ,  $y = x_0$



The minimum number count of 3-input NAND gates required to complete the design, will be

- (a) 3                                      (b) 2  
 (c) 4                                      (d) 1

6. [NAT]

How many don't care inputs are there in a BCD adder?

**Part B: 7 to 13 questions each will carry 2 marks (MCQs + NAT)**


**7. [MCQ]**

In a 4-bit carry look ahead adder, the X-OR and AND/OR gate has delay of 5ns each. The sum will appear after delay of

- (a) 10 ns (b) 20 ns  
(c) 15 ns (d) 40 ns

**8. [NAT]**

A MUX circuit is as shown below:

 


Clock input has frequency of 10 MHz, then duty cycle of the output waveform at output Y will be \_\_\_\_\_. (up to two decimal places).

 **9. The following binary values were applied to the X and Y inputs of the NAND latch shown in the figure in the sequence indicated below :**

$X = 0, Y = 1; X = 0, Y = 0; X = 1, Y = 1$


The corresponding stable P, Q outputs will be



- (a)  $P = 1, Q = 0; P = 1, Q = 0; P = 1, Q = 0$  or  $P = 1, Q = 1$   
(b)  $P = 1, Q = 0; P = 1, Q = 0$  or  $P = 0, Q = 1$  or  $P = 0, Q = 1$   
(c)  $P = 1, Q = 0; P = 1, Q = 1; P = 1, Q = 0$  or  $P = 0, Q = 1$   
(d)  $P = 1, Q = 0; P = 1, Q = 1; P = 1, Q = 1$

 **10. [MCQ]**

A MUX circuit is designed as shown below:



What is the output Y of above combinational circuit?

- (a)  $AB + BC + CA$   
(b)  $B(A + C)$   
(c)  $A \oplus B \oplus C$   
(d) Borrow output of full adder

**11. [NAT]**

A 16-bit parallel adder is designed using 16, 1-bit full adders. Each 1-bit full adder is designed using X-OR, AND and OR gates. The delay contributed by X-OR gate is 20ns while that contributed by AND/OR gate is 5ns. The number of additions per second that a 16-bit parallel adder can perform reliably, will be \_\_\_\_\_  $\times 10^6$

**12. [NAT]**


A designer has sufficient number of units of decoder with enable input of size  $4 \times 2^4$  and a decoder of size  $8 \times 2^8$  is to be realized. The number of units of  $4 \times 2^4$  decoders, required will be

13. [MCQ]

Consider the configuration of a  $2 \times 1$  MUX as shown below.

It is required to implement two variable

Boolean function  $f = P + Q$ . Then

 

- (a)  $x = Q, y = 1$  and  $z = P$
- (b)  $x = Q, y = 0$  and  $z = P$
- (c)  $x = P, y = Q$  and  $z = 0$
- (d)  $x = P, y = 0$  and  $z = Q$

## Answer Key

- |          |                                |
|----------|--------------------------------|
| 1. (5)   | 8. (0.80) [Range 0.75 to 0.82] |
| 2. (22)  | 9. (c)                         |
| 3. (a)   | 10. (b)                        |
| 4. (3)   | 11. (5.26) (Range 5.1 to 5.3)  |
| 5. (c)   | 12. (17)                       |
| 6. (312) | 13. (a)                        |
| 7. (b)   |                                |



For more questions, kindly visit the library section: Link for web: <https://smart.link/sdfez8ejd80if>



PW Mobile APP: <https://smart.link/7wwosivoicgd4>