

Weekly Test - 03

Digital Logic


Combinational Circuit


Time Duration - 50 Min
Maximum Marks - 20
Note : Negative Marking - 1/3, NAT no negative marking

{For MSQs no part marking no negative marking(from week onwards)}


Part A : 1 to 6 questions each will carry 1 marks (MCQs + NAT)

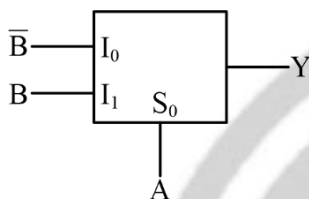1. The logic gate of given multiplexer circuit is



- (a) AND (b) X-OR
(c) XNOR (d) NAND

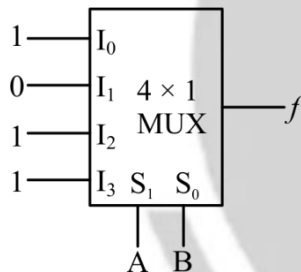2. The logic function implemented by 4×1 mux, is



- (a) $A + B$ (b) $A + \bar{B}$
(c) $\bar{A} + B$ (d) $\bar{A} + \bar{B}$

3. How many AND gates are required for a 1×8 Demux ?

4. A multiplexer with a 4-bit data select input is a

- (a) 4×1 mux (b) 16×1 mux
(c) 8×1 mux (d) 2×1 mux


5. A designer has multiplexer units of size 2×1 and multiplexer of size 16×1 is to be realized. The number of units of 2×1 mux is required will be _____.

6. How many OR gates are required for an octal to binary encoder?

- (a) 3 (b) 2
(c) 8 (d) 10


Part A : 7 to 13 questions each will carry 2 marks (MCQs + NAT)

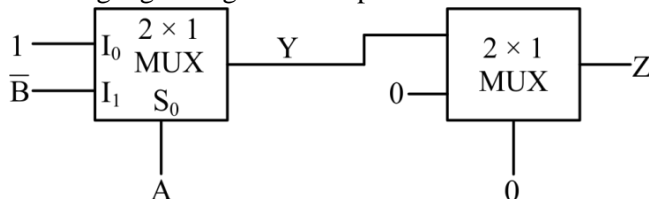7. The logic gate is given multiplexer circuit is




- (a) AND (b) XOR
(c) NAND (d) NOR

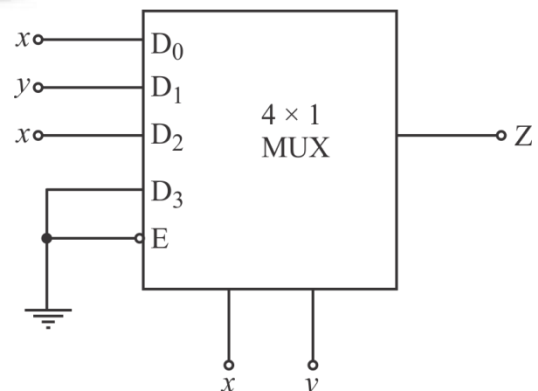8. The logic function implemented by 4×1 MUX, is



- (a) $Z = xy$ (b) $Z = x + y$
(c) $Z = x + y$ (d) $x \oplus y$

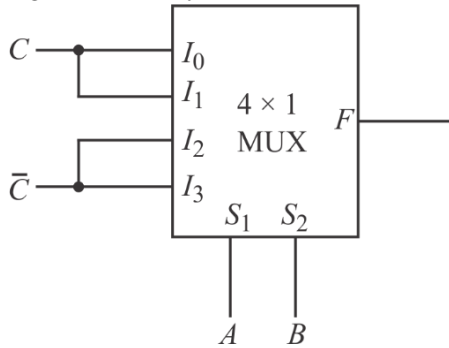9. The logic realized by the circuit shown in figure is




- (a) $F = A \odot C$ (b) $F = A \oplus C$
(c) $F = B \odot C$ (d) $F = B \oplus C$
10. Which one of the following circuits implements the Boolean function given below?

$$f(x, y, z) = m_0 + m_1 + m_3 + m_4 + m_5 + m_6$$


where m_i is the i^{th} minterm.

- (a)
- (b)
- (c)
- (d)

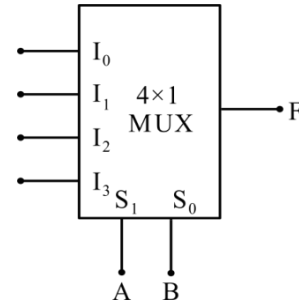
11. In the 4×1 multiplexer, the output F is given by $F = A \oplus B$. Find the required input $I_3 I_2 I_1 I_0$.



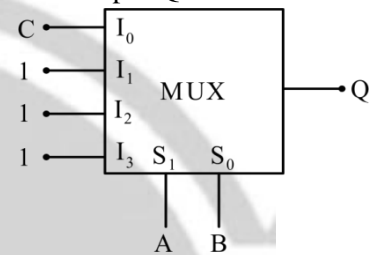- (a) 1010 (b) 0110
(c) 1000 (d) 1110
12. The combinational logic circuit shown in the given figure has an output Q which is



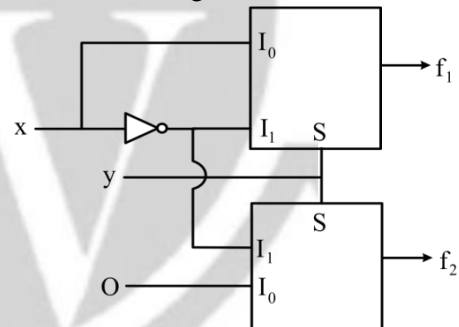- (a) ABC (b) $A + B + C$
(c) $A \oplus B \oplus C$ (d) $A \cdot B + C$
13. Minimum number of NAND gates required to implement following combinational circuit are ____.



Answer Key

- | | |
|---------|---------|
| 1. (c) | 8. (d) |
| 2. (b) | 9. (b) |
| 3. (8) | 10. (a) |
| 4. (b) | 11. (b) |
| 5. (15) | 12. (b) |
| 6. (a) | 13. (5) |
| 7. (c) | |



Hints and solutions

1. (c)

$$Y = \bar{S}_0 I_0 + S_0 I_1$$

$$Y = \bar{A} \bar{B} + AB$$



$$Y = A \odot B$$
2. (b)

$$f = 1.\bar{A}\bar{B} + 0.\bar{A}B + 1.A\bar{B} + AB.1$$

$$f = \bar{A}\bar{B} + \bar{A}B + AB$$

$$f = \bar{B} + AB = (\bar{B} + B)(\bar{B} + A)$$
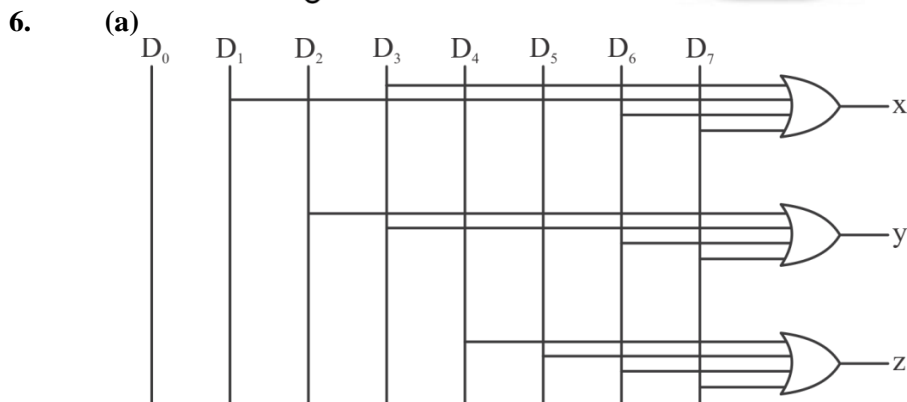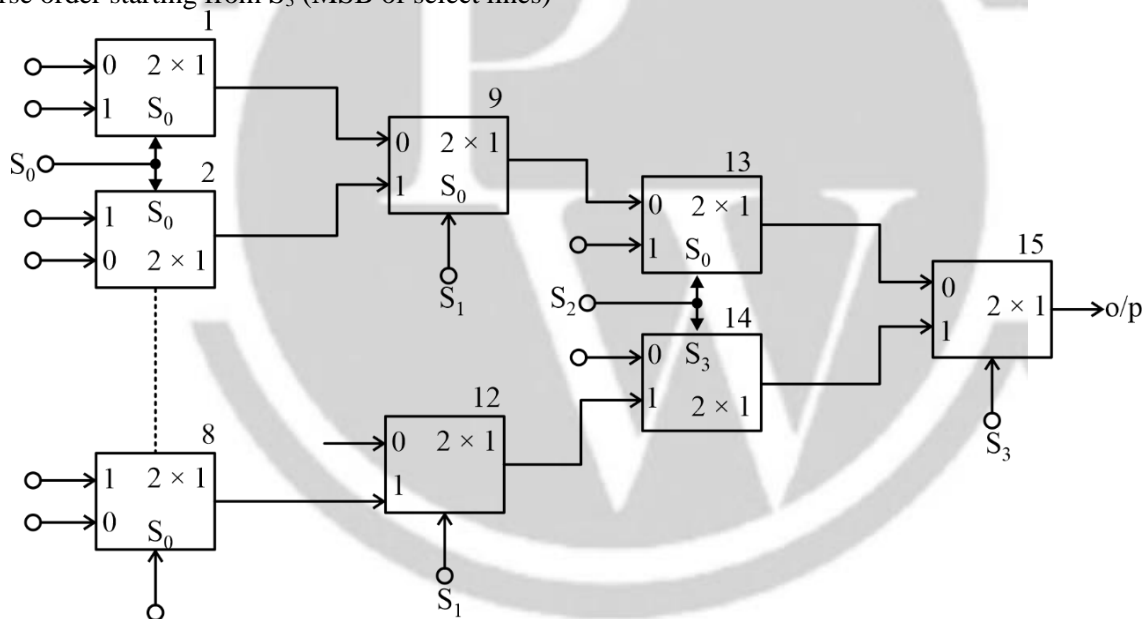
$$f = A + \bar{B}$$
3. (8)
Number of AND gates = Number of output in DEMUX
4. (b)
 16×1 mux is implemented with 4-bit data select input.
5. Number of units of 2×1 MUXs required = $8 + 4 + 2 + 1 = 15$ as demonstrated below. Select lines are assigned in reverse order starting from S_3 (MSB of select lines)



7. (c)

$$Y = \bar{A} + \bar{A}B = \bar{A} + B$$

$$Z = \bar{O}.Y + O.O$$

$$Z = Y = \bar{A} + B$$

$$Z = \overline{AB}$$

NAND Gate

8. (d)

$$z = \bar{x}y x + \bar{x}y y + \bar{x}y x + x y \cdot 0$$

$$z = \bar{x}y + x\bar{y}x$$

$$z = \bar{x}y + x\bar{y}$$

$$z = x \oplus y$$

9. (b)

$$F = \bar{A}\bar{B}C + \bar{A}BC + A\bar{B}\bar{C} + ABC$$

$$F = \bar{A}C(B + \bar{B}) + A\bar{C}(B + \bar{B})$$

$$F = \bar{A}C + A\bar{C}$$

$$F = A \oplus C$$

10. (a)

$$f = \bar{y}\bar{z} \cdot 1 + \bar{y}z \cdot 1 + y\bar{z} \cdot x + yz\bar{x}$$

$$f = x\bar{y}\bar{z} + \bar{x}\bar{y}\bar{z} + x\bar{y}z + \bar{x}\bar{y}z + xy\bar{z} + \bar{x}yz$$

$$f = \bar{x}\bar{y}\bar{z} + \bar{x}\bar{y}z + \bar{x}yz + x\bar{y}\bar{z} + x\bar{y}z + xy\bar{z}$$

$$f(x, y, z) = (m_0, m_1, m_3, m_4, m_5, m_6)$$

11. (b)

$$F = \bar{A}\bar{B}I_0 + \bar{A}BI_1 + A\bar{B}I_2 + ABI_3$$

Put $I_0 = 0, I_1 = 1, I_2 = 1, I_3 = 0$

$$F = \bar{A}B + A\bar{B}$$

$$F = A \oplus B$$

12. (b)

$$Q = \bar{A}\bar{B}C + \bar{A}B + AB\bar{C} + AB$$

$$Q = \bar{A}(\bar{B}C + B) + A(\bar{B} + B)$$

$$Q = \bar{A}(\bar{B} + B)(B + C) + A$$

$$= A(\bar{B} + C) + A$$


$$Q = (\bar{A} + A)(A + B + C)$$

$$Q = A + B + C$$

13. (5)

$$f_1 = x\bar{y} + \bar{x}y = x \oplus y$$

$$f_2 = \bar{x}y$$

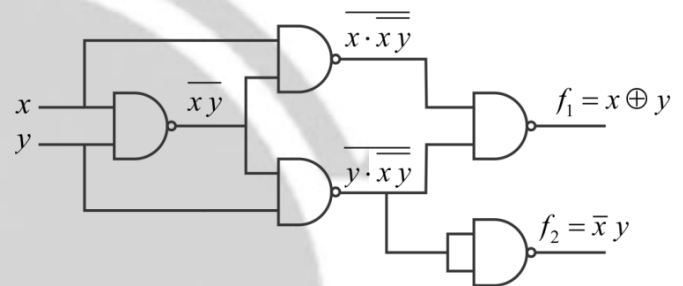

Hence 5 NAND gate required.



For more questions, kindly visit the library section: Link for web: <https://smart.link/sdfez8ejd80if>



PW Mobile APP: <https://smart.link/7wwosivoicgd4>